

Project 1 Report

Course Title: VLSI System Design

Course Code: EECE-6375

Submitted by:

Name: Md Shazarul Islam

ID: 20753526

Submitted to:

Dr. Hasina Huq

Professor, Dept. of Electrical and Computer Engineering

The University of Texas Rio Grande Valley

Table of Contents

1. Part A: Specification 2.5 (NMOS W/L)=(PMOS W/L)	3
2. Part B: Table 1	3
3. Part C: NOR Gate	4
a. Layout	
b. Input-output waveforms	
c. Inp files (Spectre simulation)	
d. Circuit Schematic	
e. Symbol	
4. Part D: NAND Gate	9
a. Layout	
b. Input-output waveforms	
c. Inp files (Spectre simulation)	
d. Circuit Schematic	
e. Symbol	
5. Part E: XOR Gate	12
a. Layout	
b. Input-output waveforms	
c. Inp files (Spectre simulation)	
d. Circuit Schematic	
e. Symbol	
6. Part F: Roadmap for Semiconductor Industry & VLSI Trends	19
7. Appendix A: NOR GATE	20
a. Rise time and Fall time	
b. Propagation Delay	
c. Area	
d. DRC	
8. Appendix B: NAND GATE	21
a. Rise time and Fall time	
b. Propagation Delay	
c. Area	
d. DRC	
9. Appendix C: XOR GATE	26
a. Rise time and Fall time	
b. Propagation Delay	
c. Area	
d. DRC	

Part A:

Specification 2.5 (NMOS W/L)=(PMOS W/L)

Explain: Why?

Ans:

Because PMOS holes are less mobile than NMOS electrons, the PMOS transistor is larger than the NMOS transistor in CMOS design. An NMOS can conduct current more effectively and switch more quickly because electron mobility is roughly two to three times greater than hole mobility. The PMOS is given a wider channel, usually two to 2.5 times the width of the NMOS, to compensate for this discrepancy and guarantee that both transistors provide an equal current drive strength. By achieving symmetrical rise and fall times during switching, this sizing contributes to stable logic levels, equal propagation delays, and effective circuit performance overall.

Part B:

TABLE 1:

Gate Type	W _n	W _p	L	RT	FT	DELAY	Frequency (GHz)	SIZE / AREA
NOR	2 μm	5 μm	180 nm (0.18 μm)	41.09ps	37.88ps	20.758ps	48.17	190.38 μm ²
NAND	2 μm	5 μm	180 nm (0.18 μm)	27.82 ps	92.34 ps	20.787ps	48.787	166.21875 μm ²
XOR	2 μm	5 μm	180 nm (0.18 μm)	79.44 ps	70.18 ps	20.767ps	48.153	842.333μm ²

Part C: NOR GATE Layout

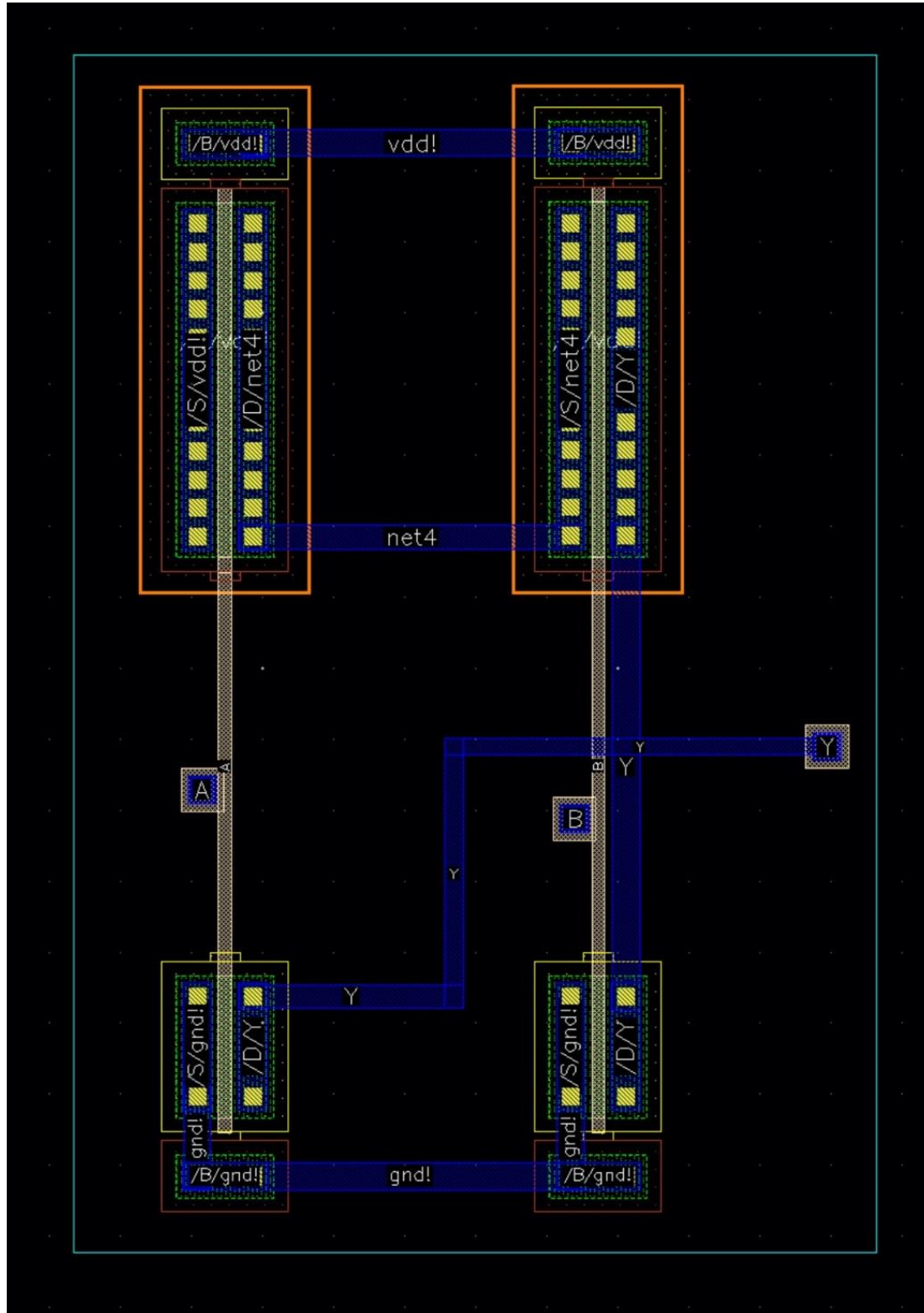


Fig.1: Layout NOR

Part C: Input-output waveforms (Truth table: 2 combinations)_NOR

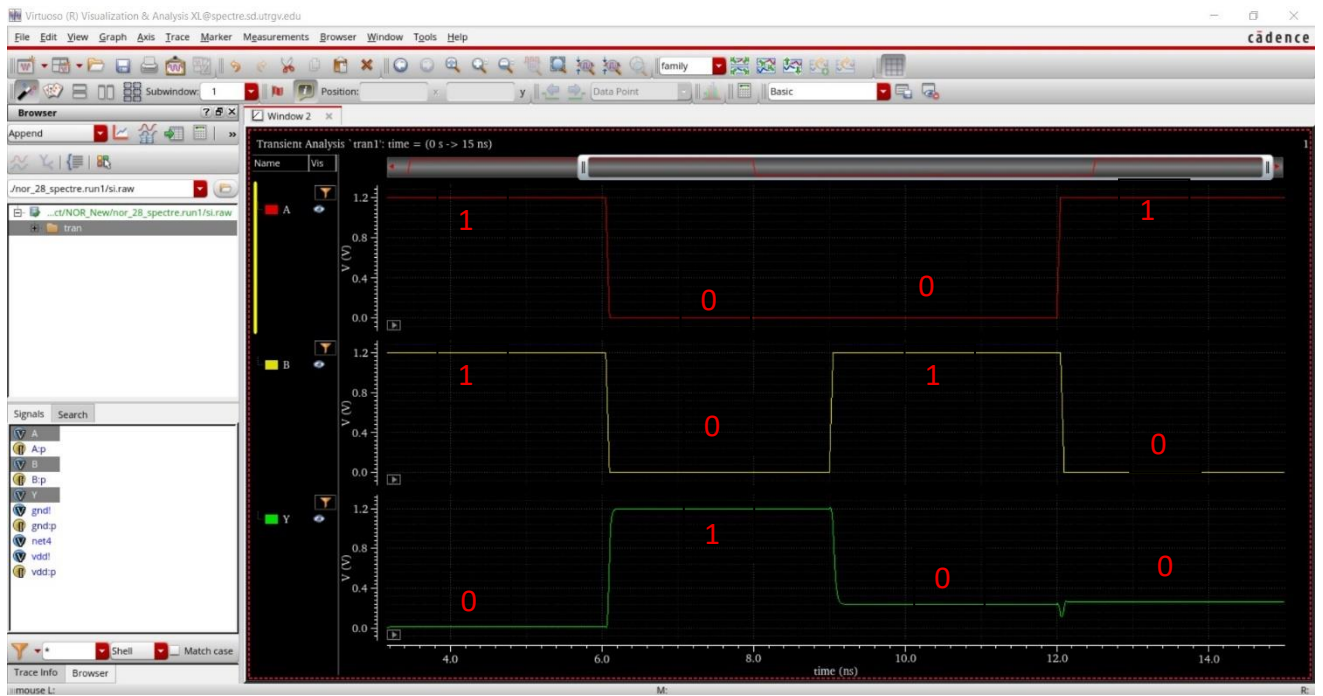


Fig.2: Input-output waveforms (Truth table: 2 combinations) of NOR Gate

Part C: Si.inp files (spectre simulation) NOR

```
// Generated for: spectre
// Generated on: Oct 28 13:42:54 2025
// Design library name: NOR_GATE
// Design cell name: NOR_GATE
// Design view name: schematic
simulator lang=spectre
global 0 vdd!

include "/home/blx188/Spectre-Models/standalone/ami06N.m"
include "/home/blx188/Spectre-Models/standalone/ami06P.m"

// Library name: NOR_GATE
// Cell name: NOR_GATE
// View name: schematic
PM1 (Y B net4 vdd!) ami06P w=(5u) l=180n as=3p ad=3p ps=11.2u pd=11.2u \
    m=(1)*(1)
PM0 (net4 A vdd! vdd!) ami06P w=(5u) l=180n as=3p ad=3p ps=11.2u pd=11.2u \
    m=(1)*(1)
NM1 (Y B 0 0) ami06N w=(2u) l=180n as=1.2p ad=1.2p ps=5.2u pd=5.2u \
    m=(1)*(1)
NM0 (Y A 0 0) ami06N w=(2u) l=180n as=1.2p ad=1.2p ps=5.2u pd=5.2u \
    m=(1)*(1)

// Spectre Source Statements
vdd (vdd! 0) vsource dc=1.2
gnd (gnd! 0) vsource dc=0
parameters vhi=1.2 tr=50p tf=50p
A (A 0) vsource type=pulse val0=0 val1=vhi rise=tr fall=tf delay=0 width=6n period=12n
B (B 0) vsource type=pulse val0=0 val1=vhi rise=tr fall=tf delay=3n width=3n period=6n
```

```

// Spectre Analyses and Output Options Statements

// Output Options
simOptions options

//+   reltol = 1.00000000E-03
//+   vabstol = 1.00000000E-06
//+   iabstol = 1.00000000E-12
//+   temp = 27
//+   save = allpub
//+   currents = selected

// Analyses

// dc1 dc oppoint=logfile homotopy=all

// tran1 tran stop=1 errpreset=moderate

tran1 tran start=0 stop=15n step=0.1n errpreset=moderate

// End of Netlist

```

Part C: Schematic NOR

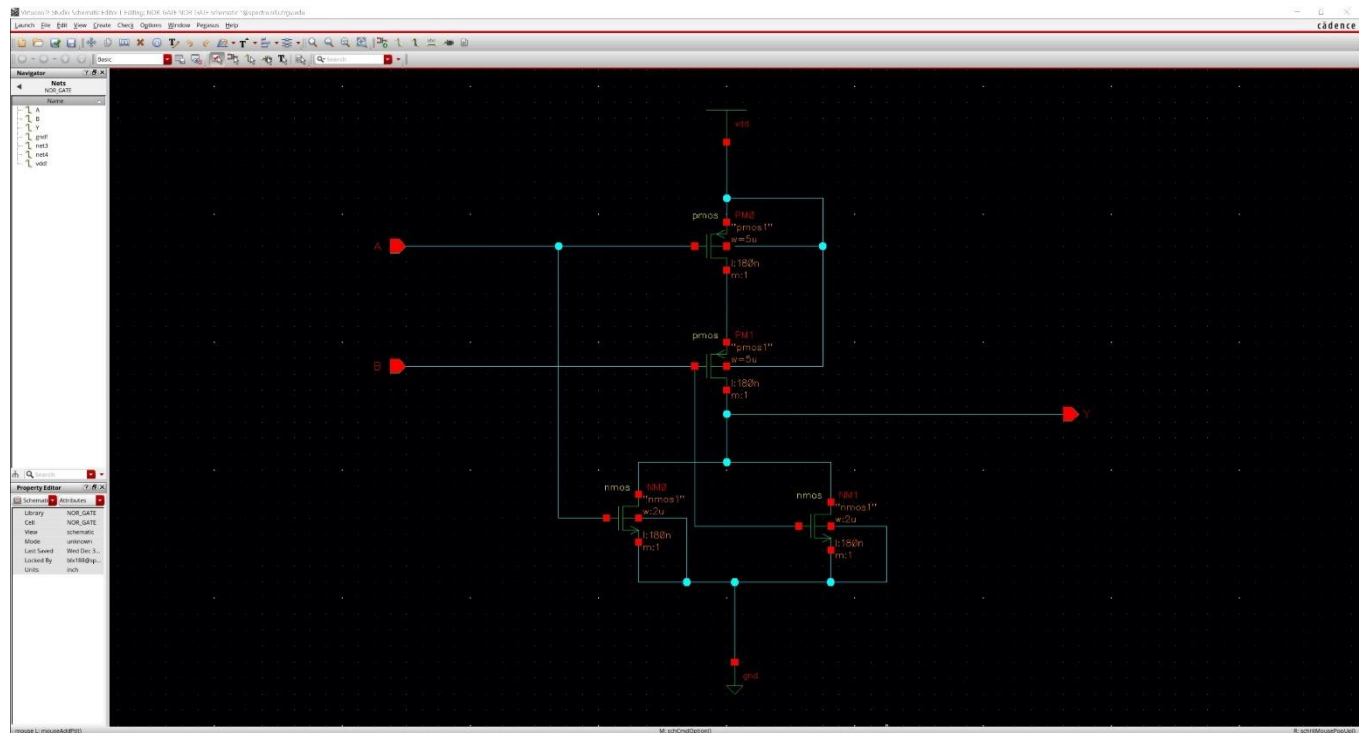


Fig.3: Circuit Schematic NOR

Part C: Symbol NOR

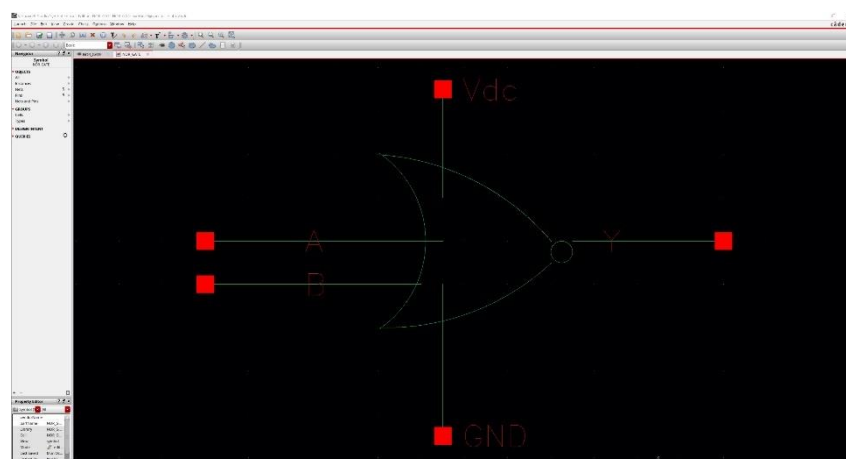


Fig.4: Symbol NOR

Part D: Layout NAND

 


Fig.5: Layout NAND

Part D: Input-output waveforms (Truth table: 4 combinations)

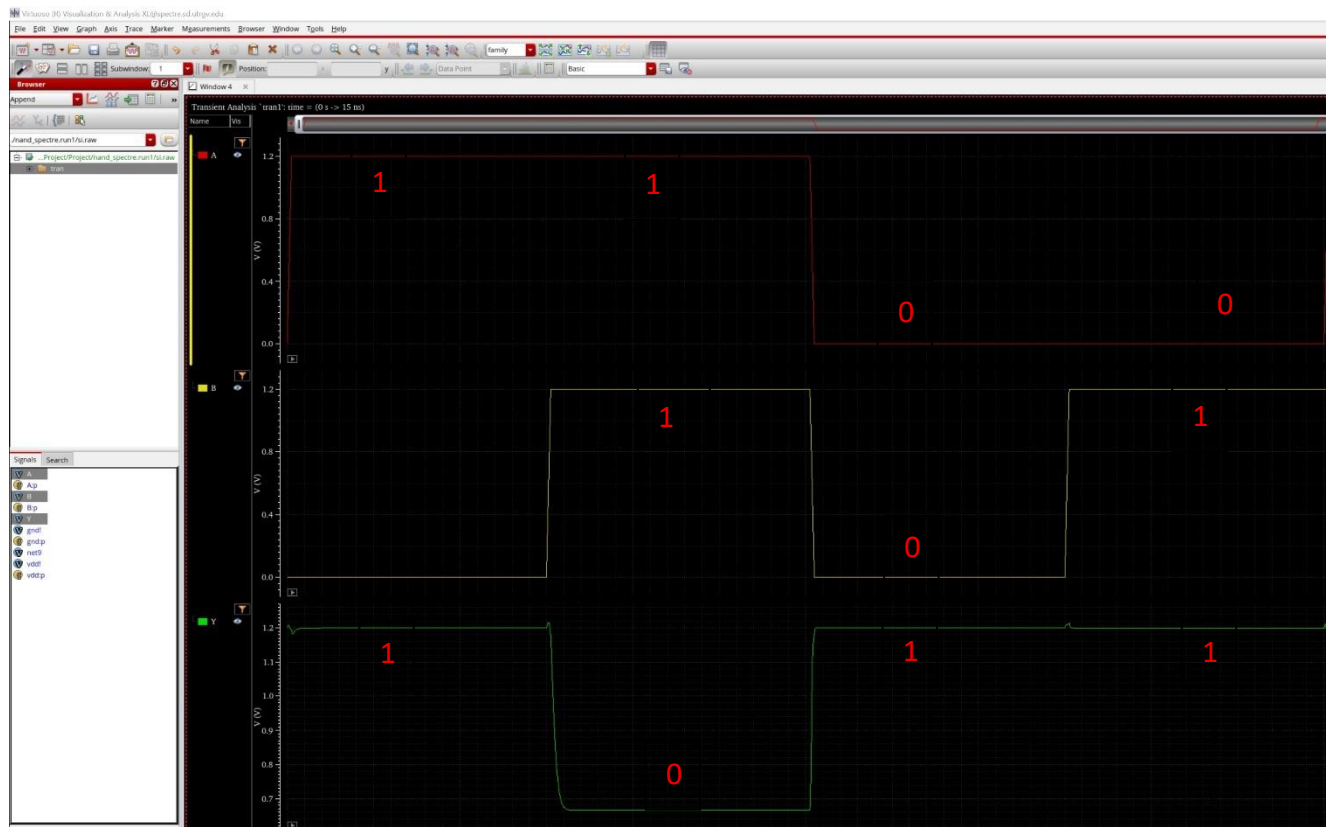


Fig.6: Simulation Output NAND

Part D: Si.inp files (spectre simulation) NAND

```
// Generated for: spectre
// Generated on: Oct 27 21:45:23 2025

// Design library name: NAND
// Design cell name: NAND_Gate
// Design view name: schematic
simulator lang=spectre

global 0 vdd!

include "/home/blx188/Spectre-Models/standalone/ami06N.m"
include "/home/blx188/Spectre-Models/standalone/ami06P.m"

// Library name: NAND
// Cell name: NAND_Gate
// View name: schematic
PM0 (Y B vdd! vdd!) ami06P w=(5u) l=180n as=3p ad=3p ps=11.2u pd=11.2u \
    m=(1)*(1)
ami06P (Y A vdd! vdd!) ami06P w=(5u) l=180n as=3p ad=3p ps=11.2u pd=11.2u \
    m=(1)*(1)
NM0 (net9 B 0 0) ami06N w=(2u) l=180n as=1.2p ad=1.2p ps=5.2u pd=5.2u \
    m=(1)*(1)
ami06N (Y A net9 0) ami06N w=(2u) l=180n as=1.2p ad=1.2p ps=5.2u pd=5.2u \
    m=(1)*(1)

// Spectre Source Statements
vdd (vdd! 0) vsource dc=1.2
gnd (gnd! 0) vsource dc=0

parameters vhi=1.2 tr=50p tf=50p
```

```

A (A 0) vsource type=pulse val0=0 val1=vhi rise=tr fall=tf delay=0 width=6n period=12n
B (B 0) vsource type=pulse val0=0 val1=vhi rise=tr fall=tf delay=3n width=3n period=6n

// Spectre Analyses and Output Options Statements

// Output Options
simOptions options

//+   reltol = 1.00000000E-03
//+   vabstol = 1.00000000E-06
//+   iabstol = 1.00000000E-12
//+   temp = 27
//+   save = allpub
//+   currents = selected

// Analyses
// dc1 dc oppoint=logfile homotopy=all
// tran1 tran stop=1 errpreset=moderate

tran1 tran start=0 stop=15n step=0.1n errpreset=moderate

// End of Netlist

```

Part D: Schematic NAND

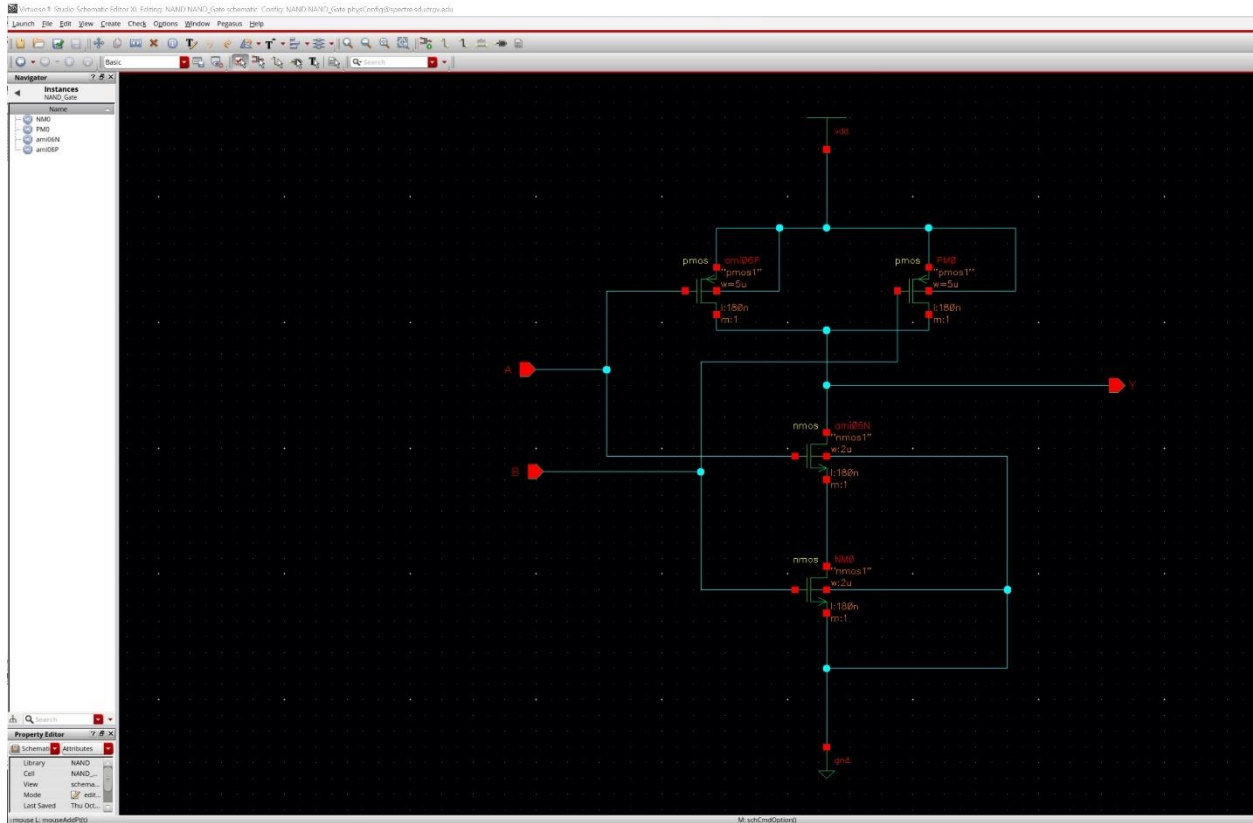


Fig.7: Schematic NAND

Part D: Symbol NAND

 


Fig.8: Symbol NAND

Part E: Layout XOR

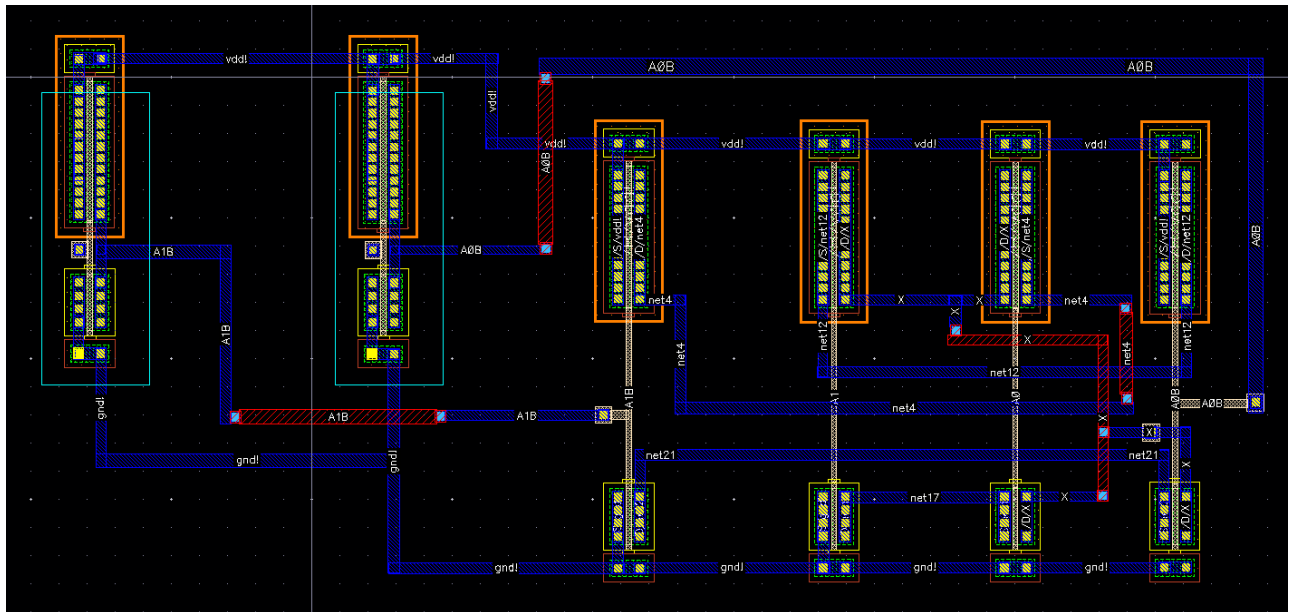


Fig.9: Layout XOR

Part E: Input-output waveforms (Truth table: 4 combinations) XOR

 


Fig.10: Input-output waveforms(XOR)

Part E: Si.inp files (spectre simulation) XOR

```
// Generated for: spectre
```

```
// Generated on: Oct 21 12:52:18 2025
```

```
// Design library name: XOR_Gate
```

```
// Design cell name: XOR_Gate
```

```
// Design view name: schematic
```

```
simulator lang=spectre
```

```
global 0 vdd!
```

```
include "/home/blx188/Spectre-Models/standalone/ami06N.m"
```

```
include "/home/blx188/Spectre-Models/standalone/ami06P.m"
```

```

// Library name: inverter_26

// Cell name: not_gate

// View name: schematic

subckt not_gate inv_in inv_out

    ami06P (inv_out inv_in vdd! vdd!) ami06P w=(5u) l=180n as=3p ad=3p \
        ps=11.2u pd=11.2u m=(1)*(1)

    ami06N (inv_out inv_in 0 0) ami06N w=(2u) l=180n as=1.2p ad=1.2p \
        ps=5.2u pd=5.2u m=(1)*(1)

ends not_gate

// End of subcircuit definition.


// Library name: XOR_Gate

// Cell name: XOR_Gate

// View name: schematic

P3 (X A1 net12 vdd!) ami06P w=(5u) l=180n as=3p ad=3p ps=11.2u pd=11.2u \
    m=(1)*(1)

P2 (net12 A0B vdd! vdd!) ami06P w=(5u) l=180n as=3p ad=3p ps=11.2u pd=11.2u \
    m=(1)*(1)

P0 (X A0 net4 vdd!) ami06P w=(5u) l=180n as=3p ad=3p ps=11.2u pd=11.2u \
    m=(1)*(1)

P1 (net4 A1B vdd! vdd!) ami06P w=(5u) l=180n as=3p ad=3p ps=11.2u pd=11.2u \
    m=(1)*(1)

N2 (net21 A1B 0 0) ami06N w=(2u) l=180n as=1.2p ad=1.2p ps=5.2u pd=5.2u \
    m=(1)*(1)

N1 (net17 A1 0 0) ami06N w=(2u) l=180n as=1.2p ad=1.2p ps=5.2u pd=5.2u \
    m=(1)*(1)

N4 (X A0B net21 0) ami06N w=(2u) l=180n as=1.2p ad=1.2p ps=5.2u pd=5.2u \
    m=(1)*(1)

```



```

N3 (X A0 net17 0) ami06N w=(2u) l=180n as=1.2p ad=1.2p ps=5.2u pd=5.2u \
    m=(1)*(1)
I0 (A1 A1B) not_gate
inverter (A0 A0B) not_gate

// Spectre Source Statements
vdd (vdd! 0) vsource dc=1.2
gnd (gnd! 0) vsource dc=0

parameters vhi=1.2 tr=5p tf=5p

// A goes low for 6 ns then high for 6 ns (period 12 ns)
A0 (A0 0) vsource type=pulse val0=0 val1=vhi rise=tr fall=tf delay=0 width=6n period=12n

// B toggles every 3 ns with period 6 ns, phased to start low then high
A1 (A1 0) vsource type=pulse val0=0 val1=vhi rise=tr fall=tf delay=3n width=3n period=6n

// Spectre Analyses and Output Options Statements

// Output Options
simOptions options

//+   reltol = 1.00000000E-03
//+   vabstol = 1.00000000E-06
//+   iabstol = 1.00000000E-12
//+   temp = 27
//+   save = allpub
//+   currents = selected

// Analyses
// dc1 dc oppoint=logfile homotopy=all
// tran1 tran stop=1 errpreset=moderate
tran1 tran start=0 stop=15n step=0.1n errpreset=moderat

// End of Netlist

```

Part E: Schematic XOR

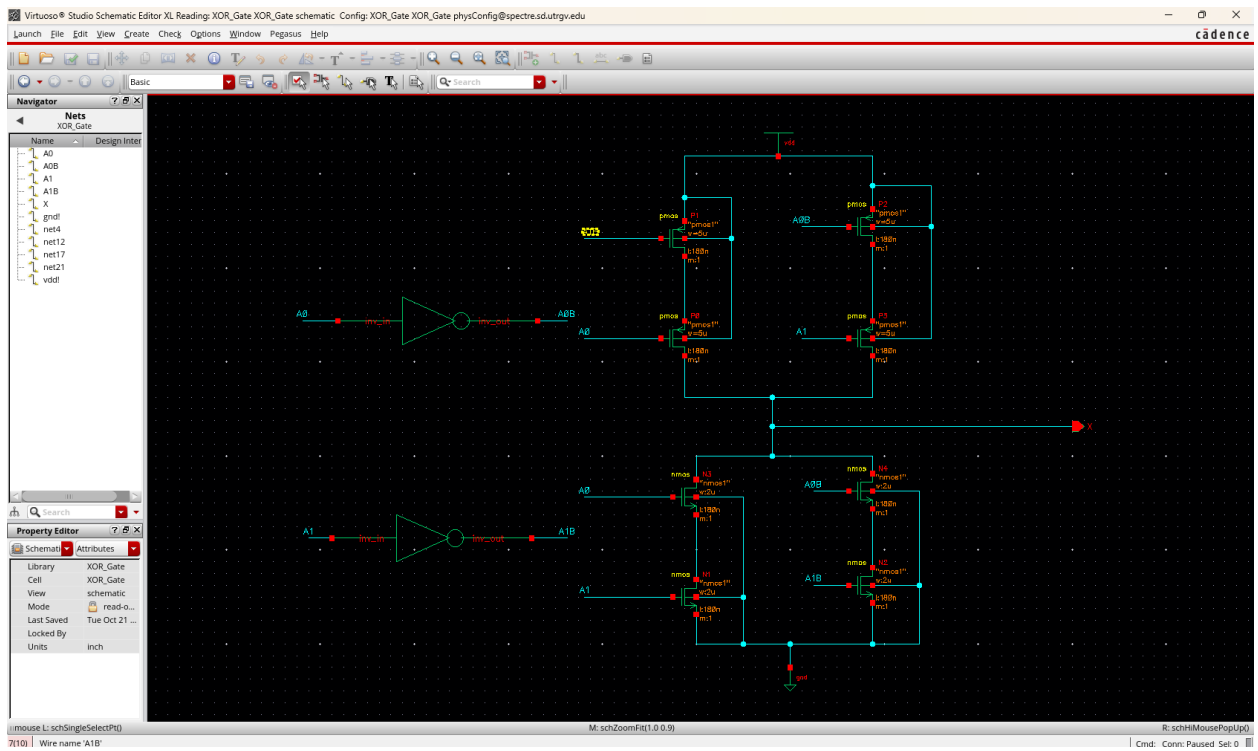


Fig.11: Circuit Schematic (XOR)

Part E: Symbol (XOR)

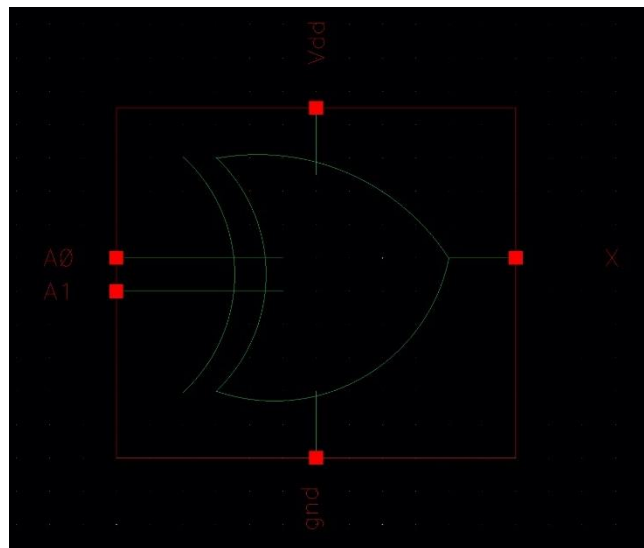


Fig.12: Symbol (XOR)

Part F: (100 words) Find a research paper (Conference papers or journal articles): Include Authors, Title, Publication year and name of the journal/conference

Topic: Roadmap for Semiconductor Industry & VLSI Trends

The paper "Semiconductor Industry: Present & Future" focuses on how the semiconductor industry is growing in the fields of AI, high-speed computing, neuromorphic computing, IoT, mobile devices, and automobiles. It illustrates the ongoing transaction from FinFET to nanosheet, optimization of power, area, and increasing the speed. As mobile, automotive, and sensor technologies advance towards greater efficiency and intelligence, advanced packaging, 3D stacking, and chip-to-chip interconnects make it possible for powerful HPC and AI systems. In the new area of VLSI, semiconductor size will be in the micro scale, will be faster, and will be more compact. In conclusion, semiconductors are about to enter a new "golden era," driving economic expansion and digital transformation as they approach a trillion-dollar global market by 2030.

Reference:

K. Zhang, "1.1 Semiconductor Industry: Present & Future," 2024 IEEE International Solid-State Circuits Conference (ISSCC), San Francisco, CA, USA, 2024, pp. 10-15, doi: 10.1109/ISSCC49657.2024.10454358.

Appendix A: NOR GATE

1. Rise Time & Fall Time of NOR gate

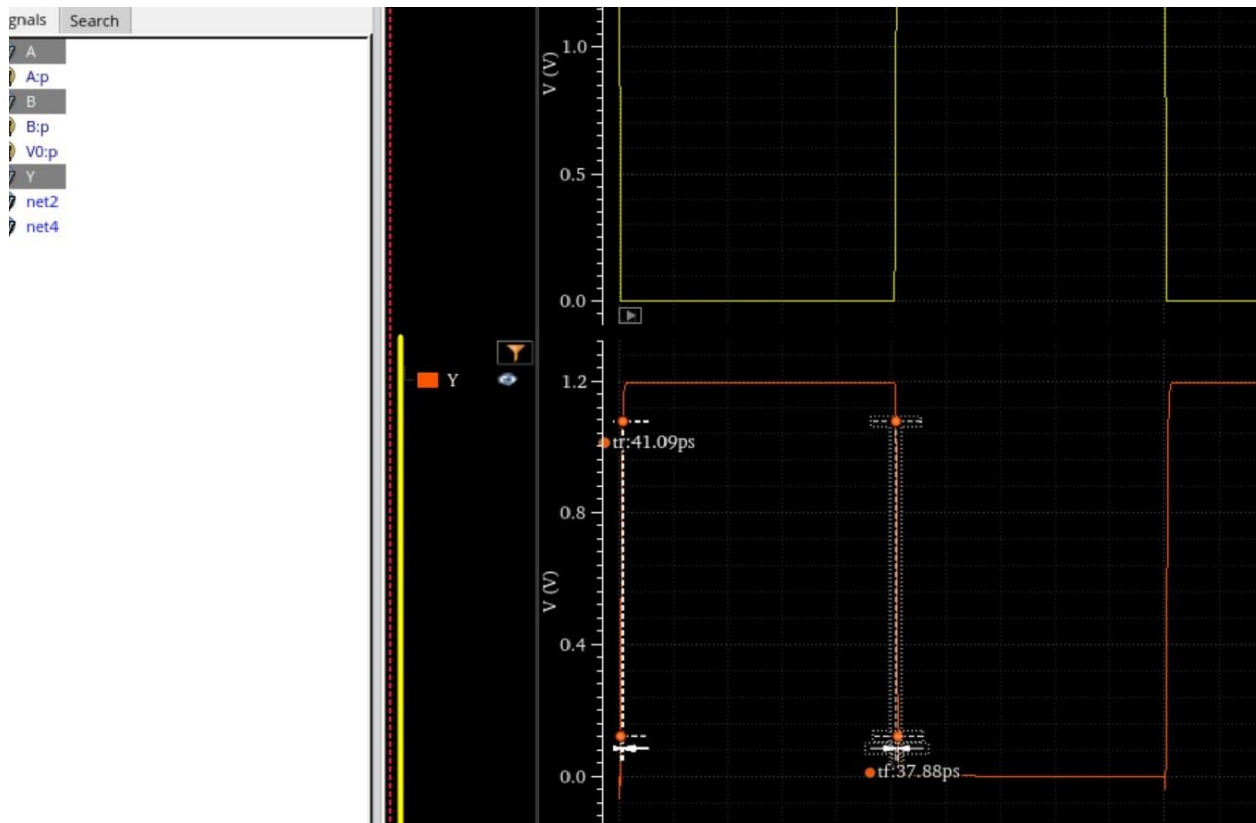


Fig.13: Rise time and Fall time (NOR)

2. Propagation Delay NOR Gate

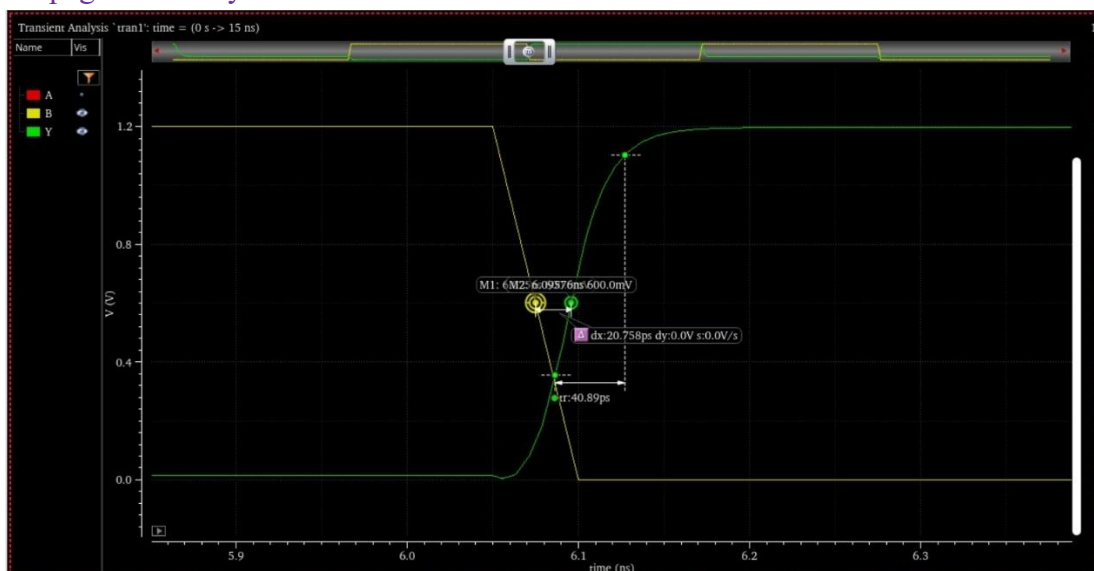


Fig.14: Propagation Delay (NOR)

3. Total Area of NOR Gate

```
❏ /tmp/areaDensity.blx188.2025Oct27_21h15m59s@spectre.sd.utrgv.edu

File Edit View Help
*****
Area and Density
*****
Library      : NOR_GATE
Cell         : NOR_gate
View         : maskLayout
Option       : current to bottom
Stop Level   : 31
Created      : UTC 2025.10.28 02:15:59.164

*****

Region       : ((2.345 -18.23) (13.64 -18.23) (13.64 -1.375) (2.345 -1.375))
TotalArea=   190.377225

Layer        : Nwell/drawing
TotalArea=   33.915000
Density=     0.178146
```

Fig.15: Area (NOR)

4. DRC Check of NOR Gate Layout

Virtuoso® Studio IC23.1 - Log: /home/blx188/CDS.log@spectre.sd.utrgv.edu

File Tools Options Help	
Dummy	nil
Flat device	nil
Master	t
Missing instance terminal	t
Name - Instances	t
Name - Nets	t
Name - Terminals	t
Net expression	nil
Opens	t
Overlapping device	nil
Parameter	t
Shorts	t
Signal type	nil
Terminal net name mismatch	t
Unbound - Instances	t
Unbound - Nets	t
Unbound - Terminals	t
Ungenerated - Instances	t
Ungenerated - Nets	t
Ungenerated - Terminals	t
NOR_GATE NOR_gate layout	
NOR_GATE NOR_gate physConfig	
NOR_GATE NOR_GATE schematic	
Checks	
	Passes Status %Clean
Complex	4 Passed 100
Connectivity - Instances	4 Passed 100
Connectivity - Terminals	3 Passed 100
Master	4 Passed 100
Missing instance terminal	4 Passed 100
Name - Instances	4 Passed
Name - Nets	6 Passed
Name - Terminals	3 Passed 100
Parameter	4 Passed 100
Terminal net name mismatch	8 Passed
Unbound - Instances	4 Passed 100
Unbound - Nets	6 Passed 100
Unbound - Terminals	3 Passed 100
Ungenerated - Instances	4 Passed 100
Ungenerated - Nets	6 Passed 100
Ungenerated - Terminals	3 Passed 100
Total	70 Passed 100
Summary	
	Total
Checks	16
Passes	16
Fails	0
Needs attention	0
%Clean	100

Fig.16: DRC Check of NOR Gate Layout

Appendix B: NAND GATE

1. Rise Time & Fall Time of the NAND gate

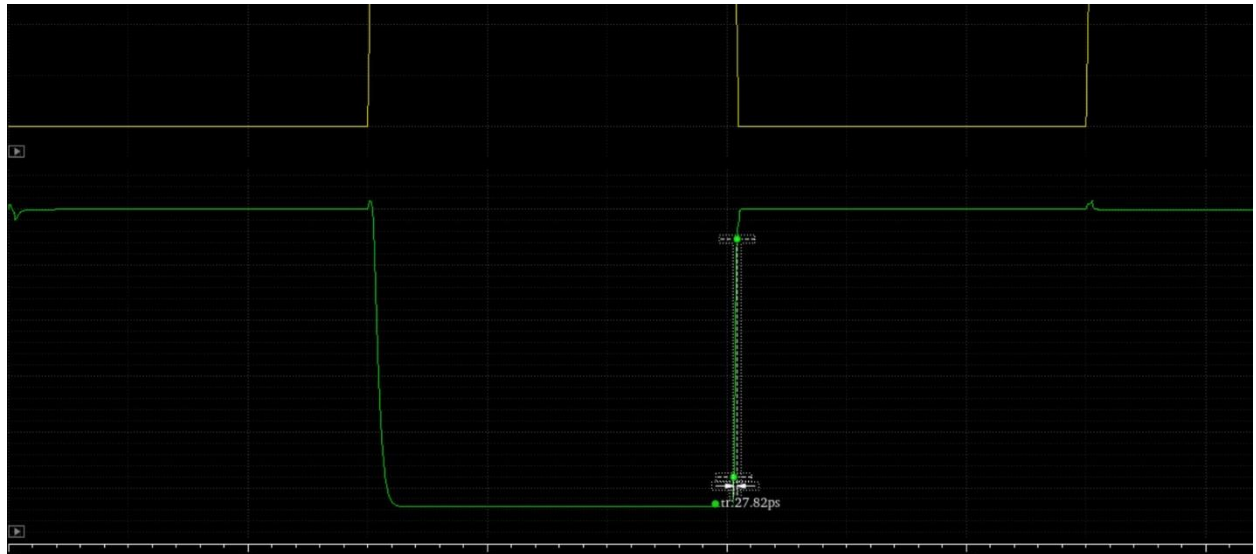


Fig.17: Rise Time

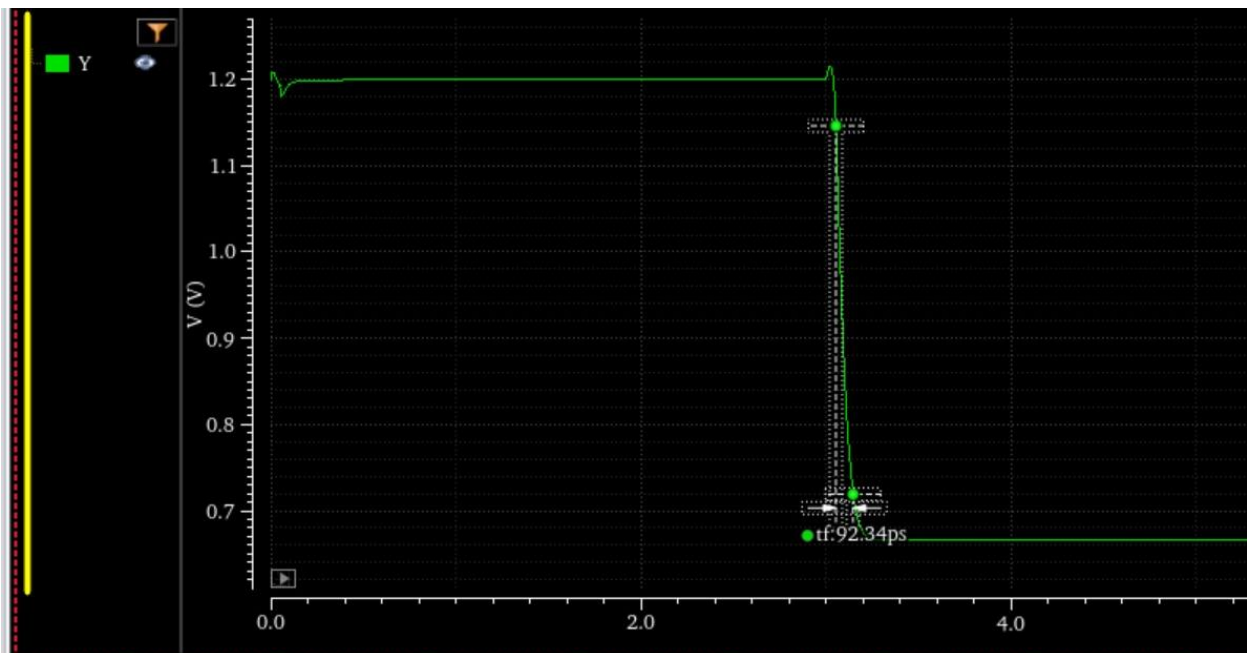


Fig.18: Fall Time

2. Propagation Delay NAND Gate

 


Fig.19: Propagation Delay NAND Gate

3. Total Area of NAND Gate

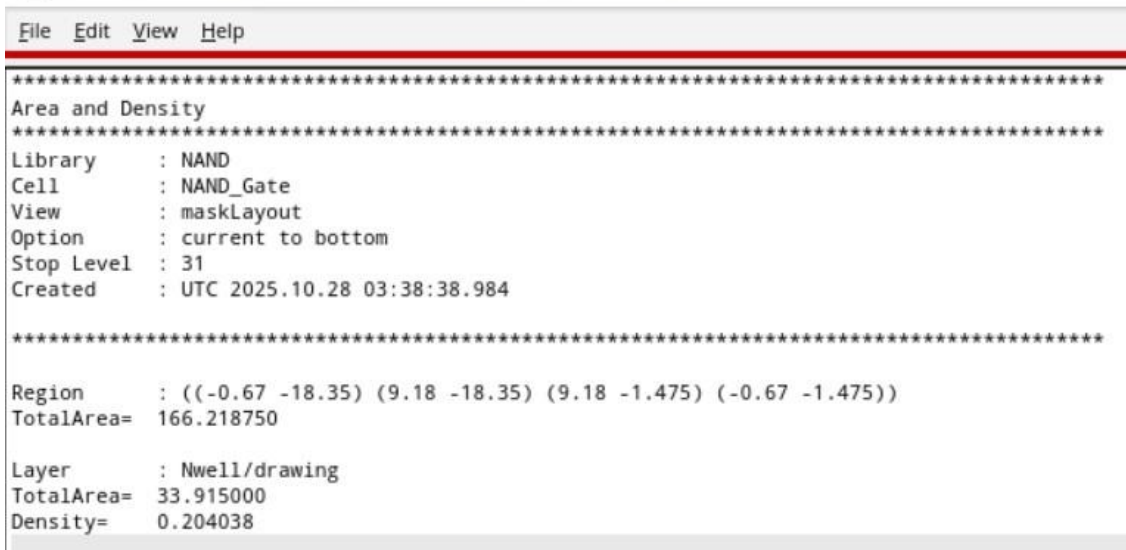

 /tmp/areaDensity.blx188.2025Oct27_22h38m38s@spectre.sd.utrgv.edu

Fig.20: Area (NAND gate)

4. DRC of NAND Gate Layout

 Virtuoso® Studio IC23.1 - Log: /home/blx188/CDS.log@spectre.sd.utrgv.edu

File	Tools	Options	Help
Dummy	nil		
Flat device	nil		
Master	t		
Missing instance terminal	t		
Name - Instances	t		
Name - Nets	t		
Name - Terminals	t		
Net expression	nil		
Opens	t		
Overlapping device	nil		
Parameter	t		
Shorts	t		
Signal type	nil		
Terminal net name mismatch	t		
Unbound - Instances	t		
Unbound - Nets	t		
Unbound - Terminals	t		
Ungenerated - Instances	t		
Ungenerated - Nets	t		
Ungenerated - Terminals	t		
NAND NAND_Gate layout			
NAND NAND_Gate physConfig			
NAND NAND_Gate schematic			
Checks			
	Passes	Status	%Clean
Complex	4	Passed	100
Connectivity - Instances	4	Passed	100
Connectivity - Terminals	3	Passed	100
Master	4	Passed	100
Missing instance terminal	4	Passed	100
Name - Instances	4	Passed	
Name - Nets	6	Passed	
Name - Terminals	3	Passed	100
Parameter	4	Passed	100
Terminal net name mismatch	8	Passed	
Unbound - Instances	4	Passed	100
Unbound - Nets	6	Passed	100
Unbound - Terminals	3	Passed	100
Ungenerated - Instances	4	Passed	100
Ungenerated - Nets	6	Passed	100
Ungenerated - Terminals	3	Passed	100
Total	70	Passed	100
Summary			
	Total		
Checks	16		
Passes	16		
Fails	0		
Needs attention	0		
%Clean	100		

Fig.21: DRC Check of NAND Gate Layout

Appendix C: XOR GATE

1. Rise Time & Fall Time of the XOR gate

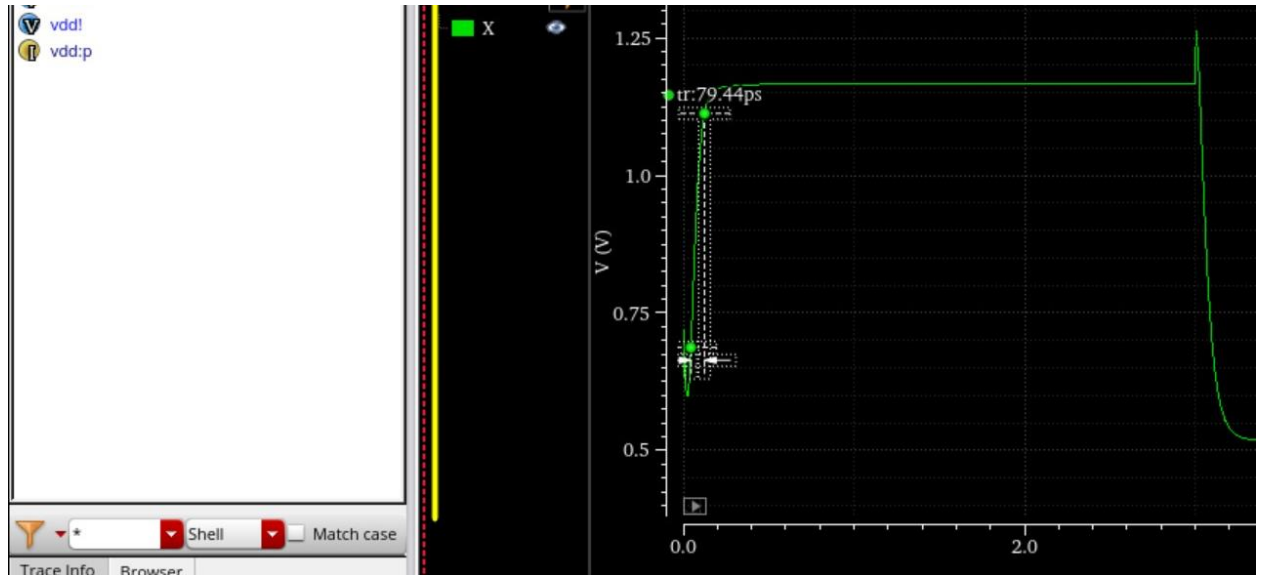


Fig.22: Rise Time

 


Fig.23: Fall Time

2. Propagation Delay NAND Gate

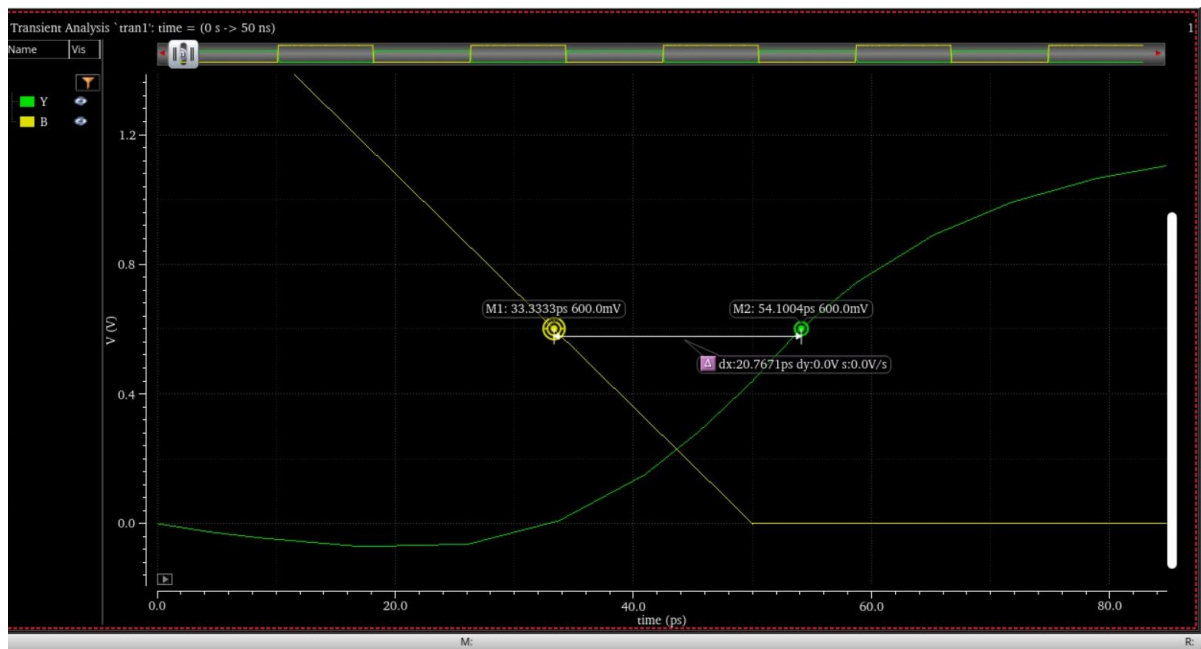


Fig.24: Propagation Delay

3. Area of XOR gate

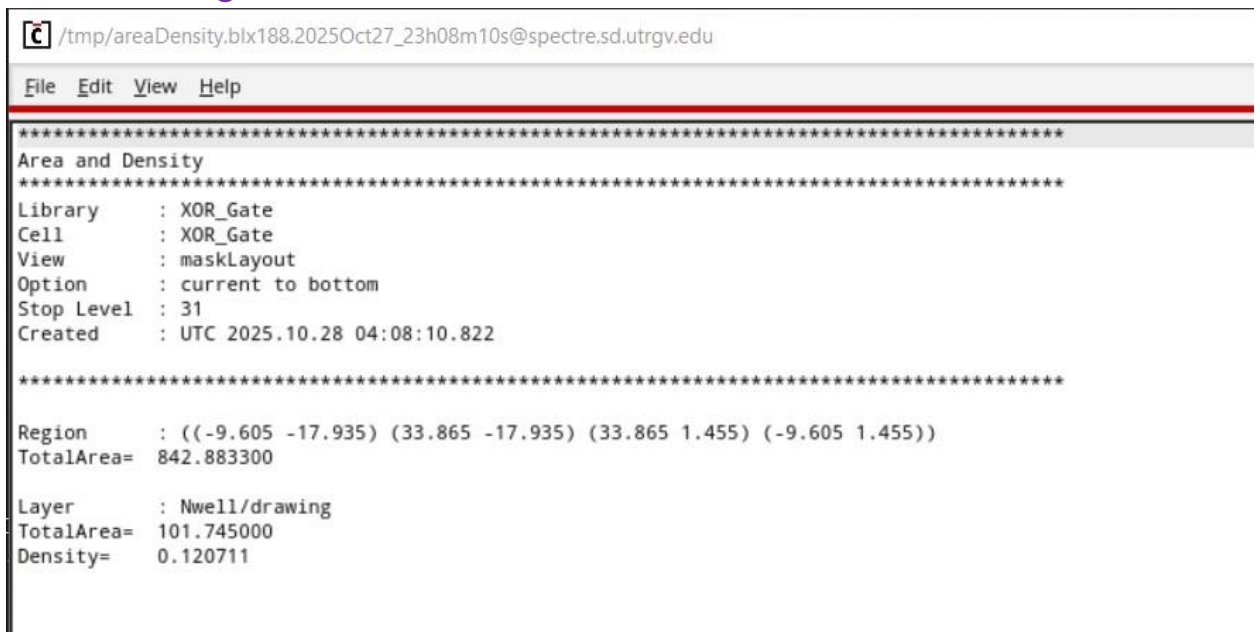


Fig.25: Area of XOR gate

4. DRC of XOR Gate Layout

Virtuoso® Studio IC23.1 - Log: /home/blx188/CDS.log@spectre.sd.utrgv.edu			
File Tools Options Help			
All cells in library	nil		
Cells without schematic	nil		
Create HTML report	t		
Open HTML report	nil		
Log file	nil		
Schematic v Layout			
Complex	t	Check	
Connectivity - Instances	t		
Connectivity - Terminals	t		
Design intent	nil		
Direction	nil		
Dummy	nil		
Flat device	nil		
Master	t		
Missing instance terminal	t		
Name - Instances	t		
Name - Nets	t		
Name - Terminals	t		
Net expression	nil		
Opens	t		
Overlapping device	nil		
Parameter	t		
Shorts	t		
Signal type	nil		
Terminal net name mismatch	t		
Unbound - Instances	t		
Unbound - Nets	t		
Unbound - Terminals	t		
Ungenerated - Instances	t		
Ungenerated - Nets	t		
Ungenerated - Terminals	t		
XOR_Gate XOR_Gate layout			
XOR_Gate XOR_Gate physConfig			
XOR_Gate XOR_Gate schematic			
Checks			
	Passes	Status	%Clean
Complex	10	Passed	100
Connectivity - Instances	10	Passed	100
Connectivity - Terminals	1	Passed	100
Master	10	Passed	100
Missing instance terminal	10	Passed	100
Name - Instances	10	Passed	
Name - Nets	11	Passed	
Name - Terminals	1	Passed	100
Parameter	10	Passed	100
Terminal net name mismatch	4	Passed	
Unbound - Instances	10	Passed	100
Unbound - Nets	11	Passed	100
Unbound - Terminals	1	Passed	100
Ungenerated - Instances	10	Passed	100
Ungenerated - Nets	11	Passed	100
Ungenerated - Terminals	1	Passed	100
Total	121	Passed	100
Summary			
	Total		
Checks	16		
Passes	16		
Fails	0		
Needs attention	0		
%Clean	100		

Fig.26: DRC of XOR Gate Layout